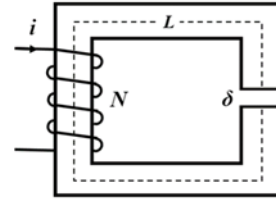


1. The magnetic circuit consists of a core material and an air-gap. The air-gap length is  $\delta$ , the core length is  $L$  and the core cross-sectional area is  $A$ . The turns of the coil are  $N$ . Assume that the core is infinite permeability ( $\mu_{Fe}=\infty$ ) and neglect the effects of magnetic leakage and fringing. Calculate: (1) the reluctance of the core  $R_{Fe}$  and that of the air-gap  $R_{\delta}$ , (2) the inductance of the coil  $L_c$ , (3) the current  $i$  required to produce an air-gap flux density  $B_{\delta}$ , (4) the corresponding flux linkage  $\Psi_c$  of the coil.



2. Draw the equivalent-T circuit of a transformer. When the primary voltage  $U_1$  increases, analyze the changes of main flux  $\Phi_m$ , core permeability  $\mu_{Fe}$ , exciting resistance  $R_m$ , exciting reactance  $X_m$  and the secondary voltage  $U_2$ .

3. A single-phase transformer with its secondary circuit open and an alternating voltage applied to its primary terminals. The core loss and exciting voltamperes were found to be  $P_{Fe}=16W$   $S=20VA$  and the primary voltage was  $U=194V$  when the winding had 200 turns. Find the power factor, the core-loss current  $I_{Fe}$ , the exciting current  $I_m$ , and the magnetizing current  $I_{\mu}$ .

4. A 50 kVA  $U_{1N}=2400V$   $U_{2N}=240V$  50Hz distribution transformer has a leakage impedance of  $0.72+j0.92 \Omega$  in the high-voltage winding and  $0.0070+j0.0090 \Omega$  in the low-voltage winding. At rated voltage and frequency, the impedance  $Z_m$  of the exciting branch (equal to the impedance of  $R_m$  and  $jX_m$  in series) is  $6.32+j43.7\Omega$  when viewed from the low-voltage side. Draw the equivalent circuit referred to (a) the high-voltage side and (b) the low-voltage side, and label the impedance numerically.

5. A 50 kVA  $U_{1N}=2400V$   $U_{2N}=240V$  50Hz distribution transformer has a leakage impedance of  $0.72+j0.92 \Omega$  in the high-voltage winding and  $0.0070+j0.0090 \Omega$  in the low-voltage winding. Find the voltage at the secondary terminals of the transformer when the load connected to its secondary draws rated current from the transformer and the power factor of the load is 0.8 **lagging**. Neglect the exciting current, and use the simplified equivalent circuit.

6. A 50 kVA  $U_{1N}=2400V$   $U_{2N}=240V$  50Hz distribution transformer has a leakage impedance of  $0.72+j0.92 \Omega$  in the high-voltage winding and  $0.0070+j0.0090 \Omega$  in the low-voltage winding. Determine the voltage regulation of the transformer operator at full load, 0.8 power factor lagging.

7. The voltage regulation of one transformer operator at full load is zero. Find that the power factor is lagging or leading.

8. With the instruments located on the high-voltage side and with the low-voltage side shorted-circuited, the short-circuit test reading for the 50 kVA  $U_{1N}=2400V$   $U_{2N}=240V$  transformer are 48V 20.8A and 617 W. An open-circuit test with the low-voltage side energized gives instrument readings on the side of 240V, 5.41A, and 186W.

Find the exciting impedance  $Z_m = R_m + jX_m$  and the short-circuit impedance  $R_k + jX_k$ . Determine the voltage regulation of the transformer operator at full load, 0.8 power factor lagging.