

### Example 1

A separately excited dc machine is operated at a constant speed of 3000r/min with a constant field current such that the emf  $E_a$  is 125V. The armature resistance  $R_a$  is  $0.02\Omega$ . Compute the armature current, terminal power and electromagnetic power and torque when the terminal voltage  $U$  is 128V.

#### Solution

In this case  $U$  is larger than  $E_a$ , and thus the machine is operating as a motor. Hence

$$I_a = (U - E_a) / R_a = (128 - 125) / 0.02 = 150 \text{ A}$$

and the power input at motor terminal is

$$P_1 = UI_a = 128 * 150 = 19.2 \text{ kW}$$

The electromagnetic power is given by

$$P_e = E_a I_a = 125 * 150 = 18.75 \text{ kW}$$

Finally, the electromagnetic torque is

$$T_e = P_e / \Omega, \Omega = 2\pi n / 60 = 2\pi * 3000 / 60 = 100\pi, T_e = 18.75 * 10^3 / (100\pi) = 59.7 \text{ N}\cdot\text{m}.$$

### Example 2

A separately excited dc machine is operated at a constant speed of 3000r/min with a constant field current such that the emf  $E_a$  is 125V. The armature resistance  $R_a$  is  $0.02\Omega$ . Compute the armature current, terminal power and electromagnetic power and torque when the terminal voltage  $U$  is 124V.

#### Solution

In this case,  $E_a$  is larger than  $U$  and hence armature current will flow out of the machine, and thus the machine is operating as a generator. Hence

$$I_a = (E_a - U) / R_a = (125 - 124) / 0.02 = 50 \text{ A}$$

and the power out at generator terminal is

$$P_2 = UI_a = 124 * 50 = 6.20 \text{ kW}$$

The electromagnetic power is given by

$$P_e = E_a I_a = 125 * 50 = 6.25 \text{ kW}$$

Finally, the electromagnetic torque is

$$T_e = P_e / \Omega, \Omega = 2\pi n / 60 = 2\pi * 3000 / 60 = 100\pi, T_e = 6.25 * 10^3 / (100\pi) = 19.9 \text{ N}\cdot\text{m}.$$

### Example 3

A separately excited dc machine is operated at a constant speed of 3000r/min with a constant field current such that the emf  $E_a$  is 125V. The armature resistance  $R_a$  is  $0.02\Omega$ . The machine is observed to be operating as a motor with a terminal voltage  $U$  of 123 V and with an input terminal power of 21.9 kW. Calculate the speed of the motor.

#### Solution

The armature current can be found from the terminal voltage  $U$  and power as

$$I_a = P_1 / U = 21900 / 123 = 178 \text{ A}$$

Thus the emf  $E_a$  is

$$E_a = U - I_a R_a = 119.4 \text{ V}$$

Because  $E_a = C_e \Phi n$ , then the rotational speed can be found as

$$n = n_0 * E_a / E_{a0} = 3000 * 119.4 / 125 = 2866 \text{ r/min}$$

#### Example 4

A permanent-magnet dc motor without field winding is known to have an armature resistance of  $1.03 \Omega$ . When operated at no load from a dc source 50V, it is observed to rotate at a speed of 2100 r/min and to draw a current of 1.25A. Find (a) The  $C_e \Phi$  (b) the no-load rotational losses of the motor, and (c) the power output of the motor when it is operating at 1700 r/min from a 48V source.

#### Solution

a. The emf  $E_a$  can be found as

$$E_a = U - I_a R_a = 50 - 1.25 \times 1.03 = 48.7 \text{ V}$$

At a speed of 2100 r/min

$$E_a = C_e \Phi n \quad C_e \Phi = E_a / n = 48.7 / 2100 = 0.0232 \text{ V} \cdot (\text{min/r})$$

b. At no load, all the electromagnetic power  $P_e$  is used to supply rotational losses. Therefore

$$P_0 = P_e - P_2 = P_e = E_a I_a = 48.7 \times 1.25 = 60.87 \text{ W}$$

$$T_0 = P_0 / \Omega = 60.87 / (6.28 \times 2100 / 60) = 0.277 \text{ N} \cdot \text{m}$$

c. At 1700r/min

$$E_a = C_e \Phi n = 0.0232 \times 1700 = 39.44 \text{ V}$$

The armature current can be found as

$$I_a = (U - E_a) / R_a = (48 - 39.44) / 1.03 = 8.31 \text{ A}$$

The electromagnetic power  $P_e$  can be calculated as

$$P_e = E_a I_a = 39.44 \times 8.31 = 327.74 \text{ W}$$

Assuming the no-load Torque  $T_0$  to be constant at their no-load value (certainly an approximation), the output shaft power  $P_2$  can be calculated:

$$P_0 = T_0 \Omega = 0.277 \times 6.28 \times 1700 / 60 = 49.29 \text{ W}$$

$$P_2 = P_e - P_0 = 327.74 - 49.29 = 278.45 \text{ W}$$