
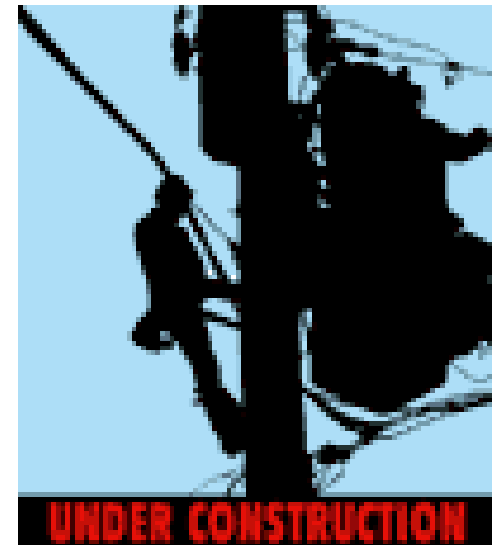


Transformer

Dr. Luo Ciyong

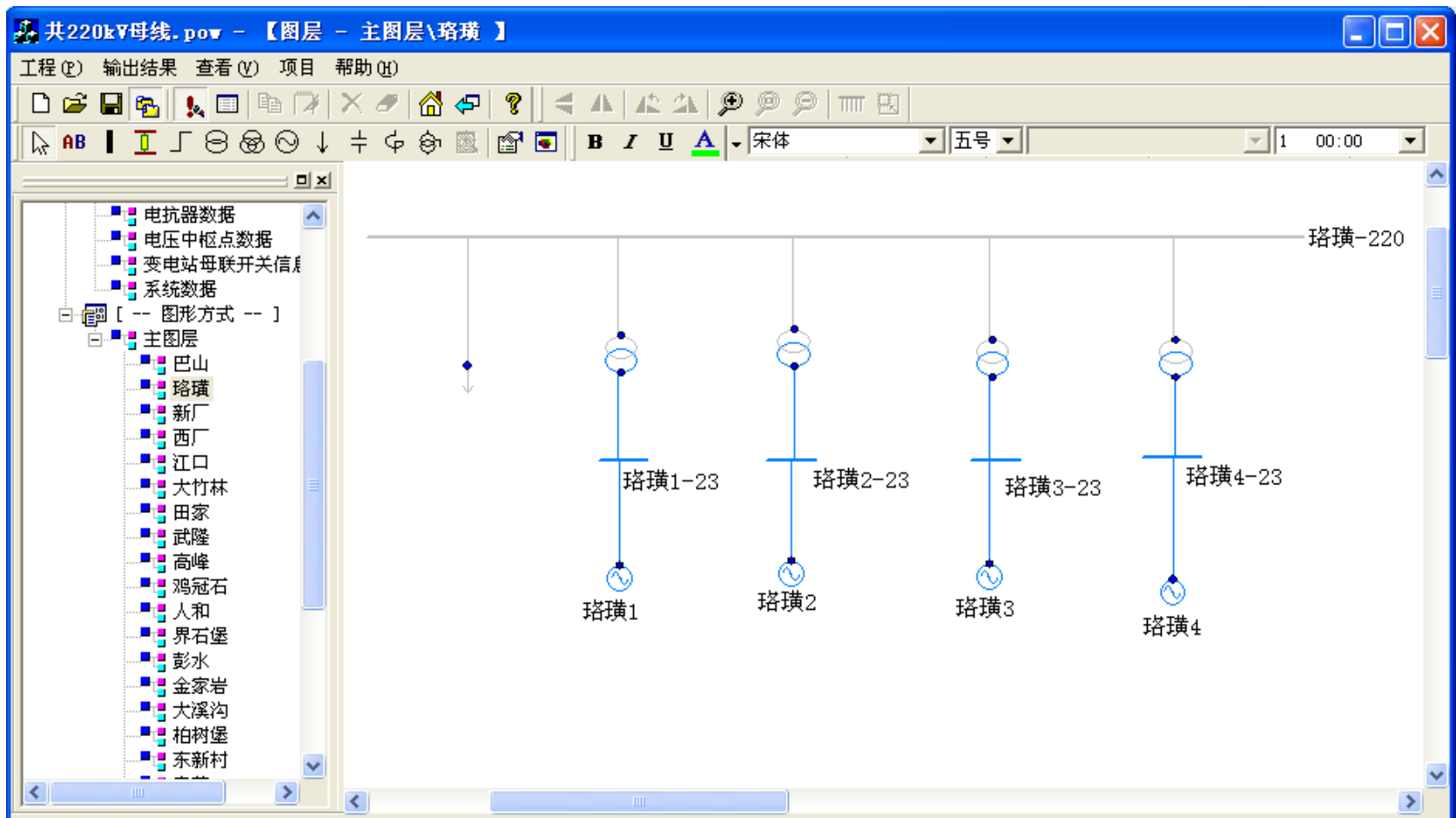



Transformer:


An electromagnetic device that changes ac electric power from one voltage level to another voltage level by the action of magnetic coupling.





SG(H)B10- Transformer

Structures

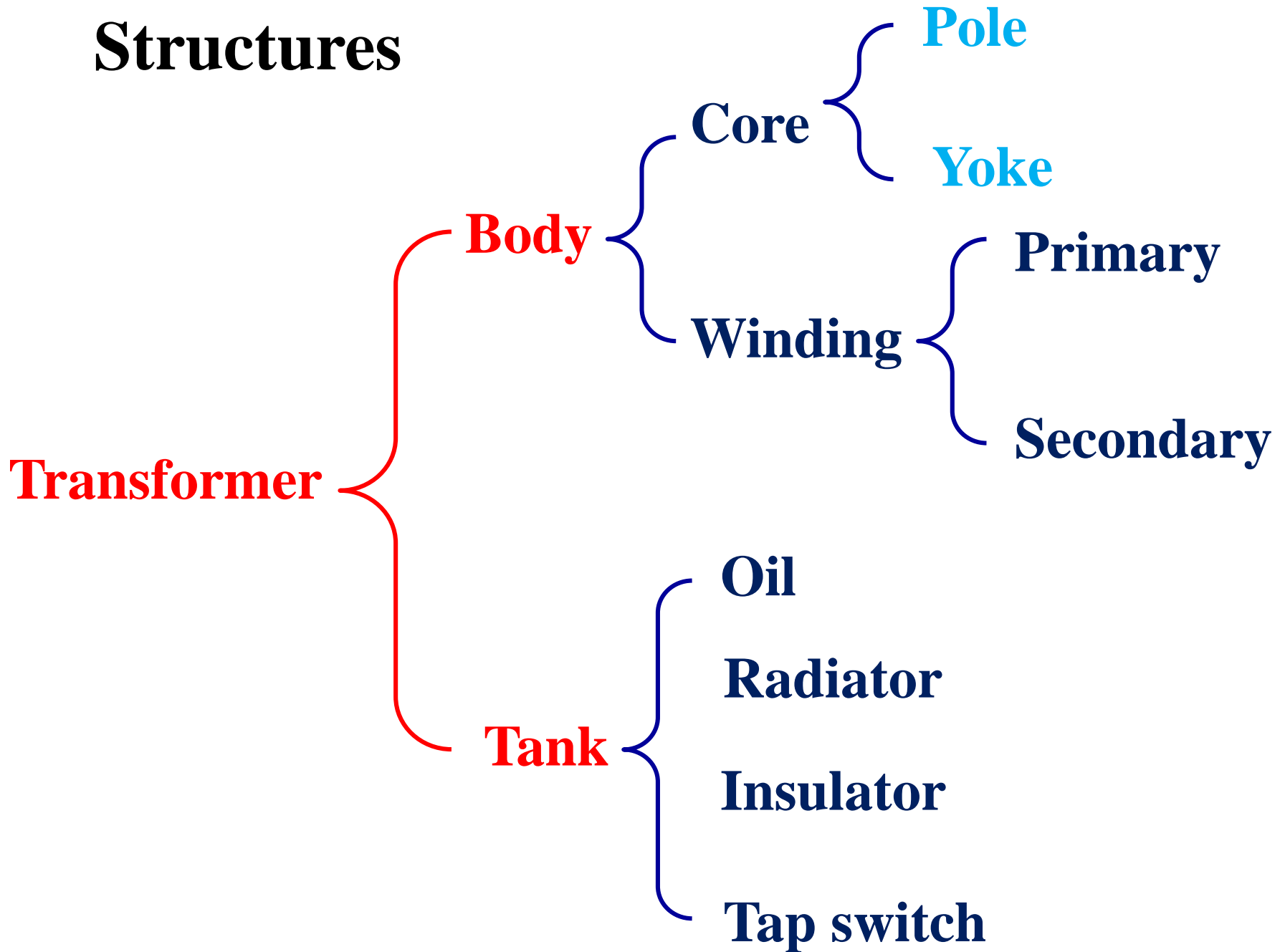

Rated values

Rated values : under these operation parameters , the apparatus is safety, reliable and has good performances, such as high efficiency, et al.

$$f_N, S_N, U_{1N}, U_{2N}, I_{1N}, I_{2N}$$

U_{2N} : : When the rated voltage U_{1N} is applied to the primary and **the secondary is open**, the voltage between any two phase of the secondary is the secondary rated voltage. $U_{2N}=U_{20}$

Single Phase:

$$S_N = U_{1N} \times I_{1N} = U_{2N} \times I_{2N}$$


Three Phase:

$$S_N = \sqrt{3} \times U_{1N} \times I_{1N} = \sqrt{3} \times U_{2N} \times I_{2N}$$

No-load Operation

The primary is connected to ac voltage source, and the secondary is open.

Positive direction

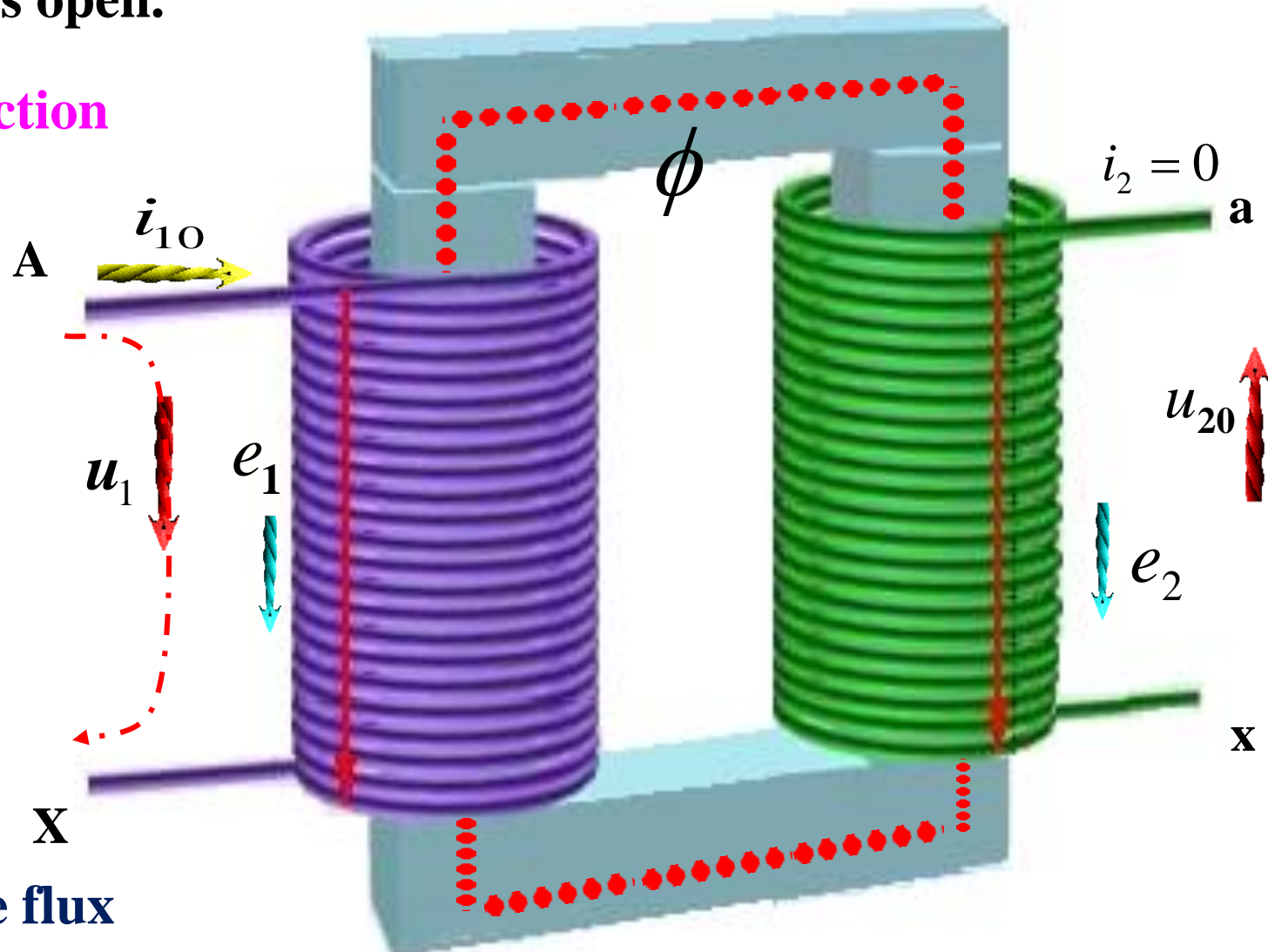

Ignore leakage flux

No-load Operation

$$e_1 = -N_1 \frac{d\phi}{dt}$$

$$e_2 = -N_2 \frac{d\phi}{dt}$$

$$\frac{e_1}{e_2} = \frac{N_1}{N_2}$$

$$u_1 = i_{10}R_1 + (-e_1) = i_{10}R_1 + N_1 \frac{d\phi}{dt}$$

$$u_{20} = e_2 = -N_2 \frac{d\phi}{dt}$$

$$\left| \frac{u_1}{u_{20}} \right| \approx \frac{e_1}{e_2} = \frac{N_1}{N_2} = k$$

No-load Operation

$$\dot{U}_1 \longrightarrow \dot{I}_0 \longrightarrow \dot{F}_0 = N_1 \dot{I}_0 \longrightarrow \dot{\Phi}_0 \longrightarrow \begin{pmatrix} \dot{E}_1 \\ \dot{E}_2 \end{pmatrix}$$

$$\dot{U}_1 = \dot{I}_{10} R_1 - \dot{E}_1 \approx -\dot{E}_1$$

$$\dot{E}_2 = \dot{U}_{20}$$

No-load Operation

Assume: The Voltage source u_1 is sinusoidal wave.

$$u_1 \approx -e_1 \quad e_1 = \sqrt{2}E_1 \sin \omega t$$

$$\phi = -\frac{1}{N_1} \int e_1 dt = -\frac{1}{N_1} \int \sqrt{2}E_1 \sin \omega t dt$$

$$= \frac{\sqrt{2}E_1}{\omega N_1} \cos \omega t = \frac{\sqrt{2}E_1}{2\pi f N_1} \cos \omega t$$

$$= \frac{E_1}{4.44 f N_1} \cos \omega t = \Phi_m \cos \omega t \quad U_1 \approx E_1 = 4.44 f N_1 \Phi_m$$

Conclusion:

The waveform and the amplitude of the main flux are determined by those of the voltage source.

No-load Operation

$$U_1 \approx E_1 = 4.44 f N_1 \Phi_m$$

When $U_1=C$: $f \nearrow \rightarrow \Phi_m \searrow \rightarrow \text{Saturation} \searrow \rightarrow \mu_{Fe} \nearrow$

When $f=C$: $U_1 \nearrow \rightarrow \Phi_m \nearrow \rightarrow \text{Saturation} \nearrow \rightarrow \mu_{Fe} \searrow$

Discussion: There are two identical transformers which are all same except their frequencies are 50Hz and 60Hz respectively, represent A and B. In the case of consideration of saturation, please compare the no-load loss and no-load current.

Analysis: The two transformers are all same except their frequencies are 50Hz and 60Hz respectively.

$f \uparrow \rightarrow \Phi_m \downarrow \rightarrow B_m \downarrow$ when $U_1 = 4.44 f N_1 \Phi_m = C$.

Because $p_{Fe} = C_{Fe} f^{1.3} B_m^2 G$, this leads to $p_{Fe} \downarrow$.


On the other hand, with $p_{Fe} \downarrow$, the exciting resistance $R_m \downarrow$ (R_m represents core loss). With $B_m \downarrow$, core saturation \downarrow and $\mu_{Fe} \uparrow$.

Because $X_m = 2\pi f L_m = 2\pi f N^2 \mathcal{A}_m = 2\pi f N^2 (\mu_{Fe} A / L)$, when $f \uparrow$ and $\mu_{Fe} \uparrow$, $X_m \uparrow$. This leads to $Z_m \uparrow$ and $I_m \downarrow$.


Exciting Current

$$\dot{I}_{10} = \dot{I}_m$$
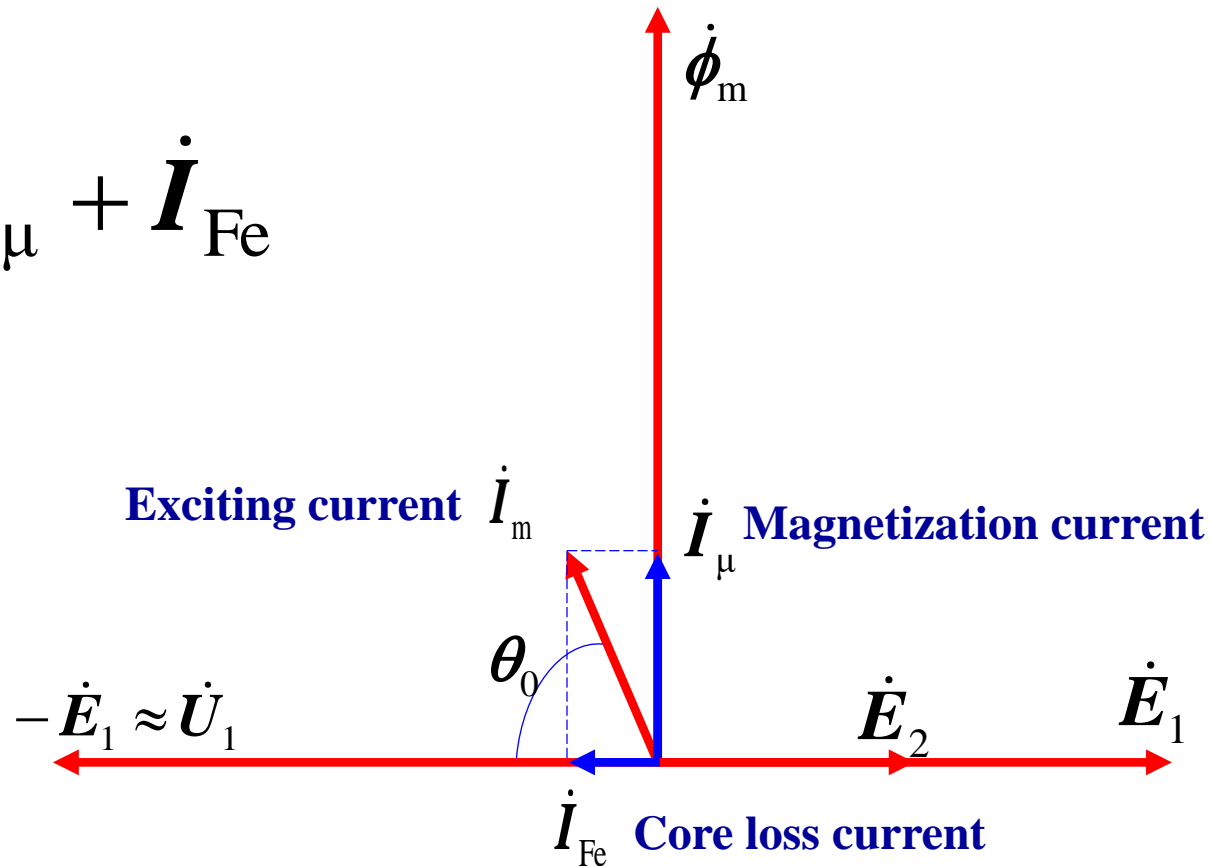
$$\dot{I}_m = \dot{I}_\mu + \dot{I}_{\text{Fe}}$$



Saturation

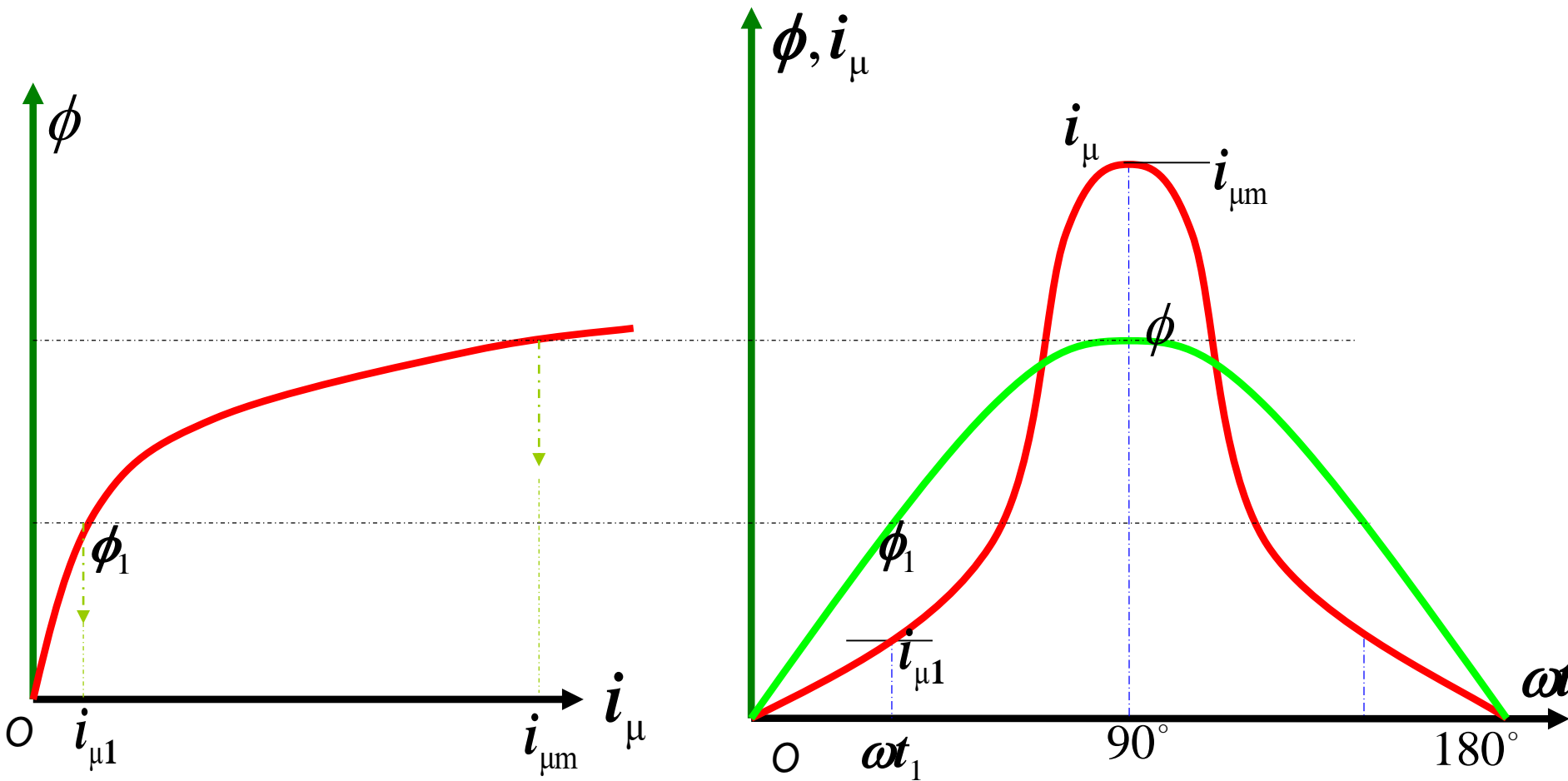

Exciting impedance

Mathematical modeling

$$\begin{aligned}\phi &= N_1 i_\mu \cdot \Lambda_m \\ e_1 &= -N_1 \frac{d\phi}{dt} = -N_1 \frac{d(N_1 i_\mu \cdot \Lambda_m)}{dt} \\ &= -N_1^2 \Lambda_m \frac{di_\mu}{dt} = -L_{1\mu} \frac{di_\mu}{dt}\end{aligned}$$

$$\dot{E}_1 = -j\omega L_{1\mu} \dot{I}_\mu = -jX_\mu \dot{I}_\mu$$

$$\dot{I}_\mu = -\frac{\dot{E}_1}{jX_\mu}$$

$$X_\mu = \omega L_{1\mu} = \omega N_1^2 \Lambda_m$$



Magnetizing reactance

Exciting impedance

Mathematical modeling

$$p_{\text{Fe}} \propto E_1^2 \quad \Rightarrow \quad p_{\text{Fe}} = \frac{E_1^2}{R_{\text{Fe}}}$$




$$\dot{E}_1 = -\dot{I}_{\text{Fe}} R_{\text{Fe}}$$

$$\dot{I}_{\text{Fe}} = -\frac{\dot{E}_1}{R_{\text{Fe}}}$$

R_{Fe} Core loss resistance

$$\dot{\mathbf{I}}_{\text{m}} = \dot{\mathbf{I}}_{\mu} + \dot{\mathbf{I}}_{\text{Fe}}$$

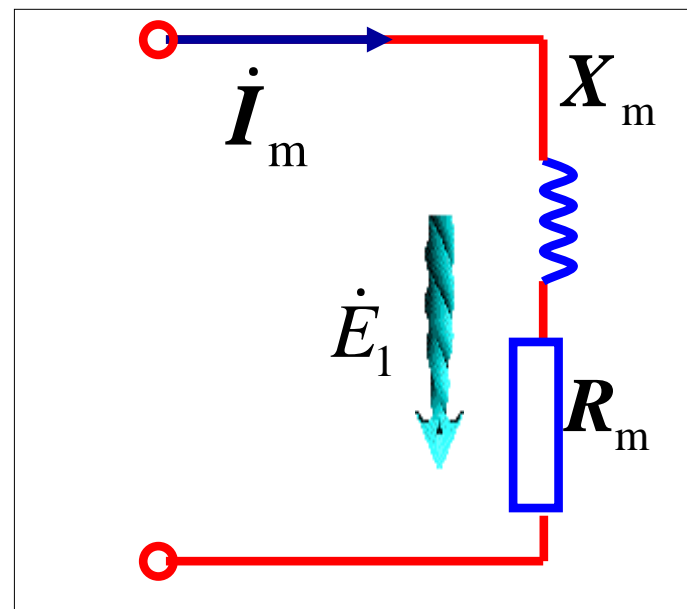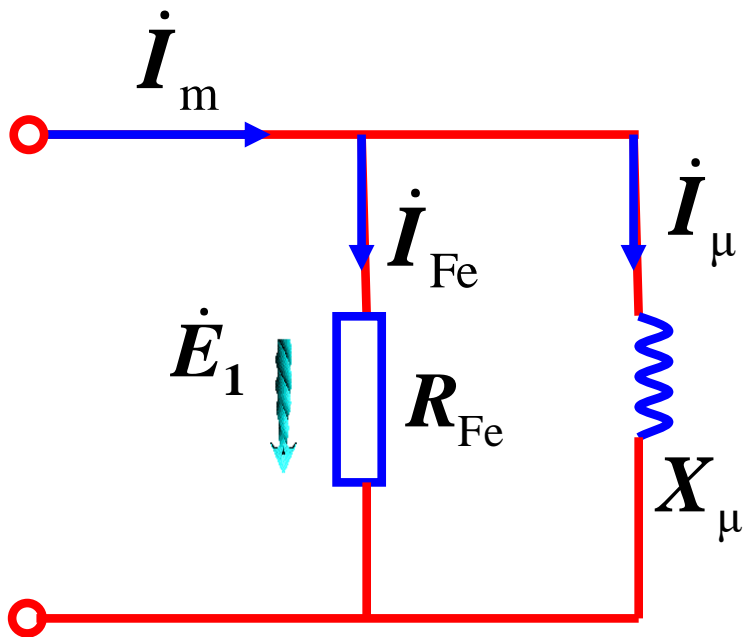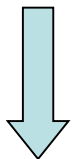
$$\dot{\mathbf{E}}_1 = -\dot{\mathbf{I}}_{\text{Fe}} \mathbf{R}_{\text{Fe}} \quad \dot{\mathbf{E}}_1 = -j\mathbf{X}_{\mu} \dot{\mathbf{I}}_{\mu}$$



$$\dot{\mathbf{E}}_1 = -\dot{\mathbf{I}}_{\text{m}} \mathbf{Z}_{\text{m}}$$

Load Operation

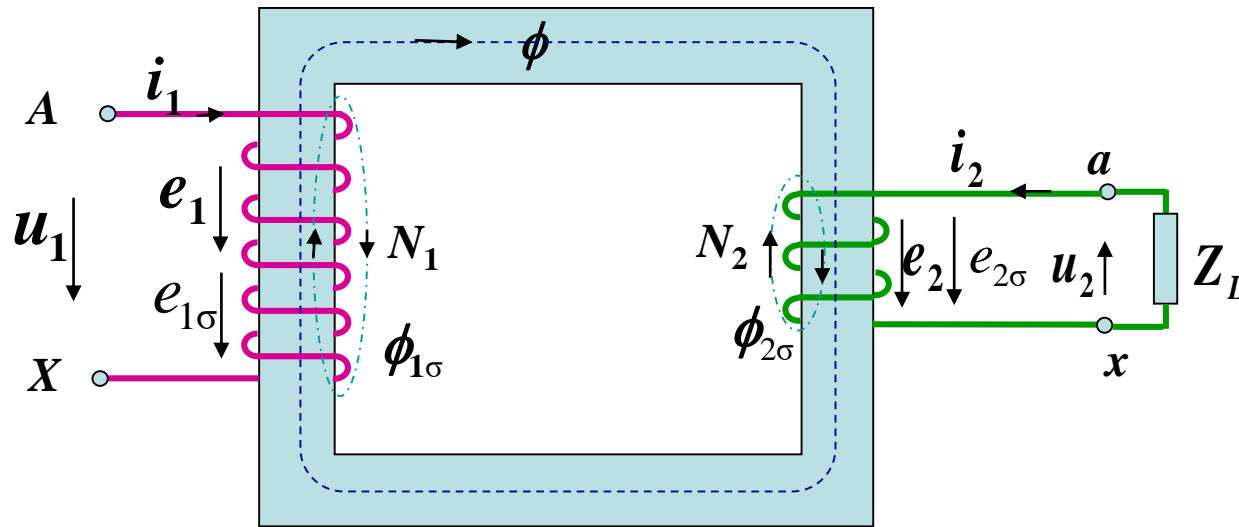The primary is connected to ac voltage source, and the secondary is closed by a load impedance.



Load Operation

$$U_1 \approx E_1 = 4.44 f N_1 \Phi_m \quad \Phi_m \text{ changes almost nothing.}$$

No-load: $i_{10}=i_m \quad F_{10}=F_m=N_1 i_m$

Load: $i_1=i_m+i_{1L}$

MMF of primary: $F_1=N_1 i_m+N_1 i_{1L}$.

MMF of Secondary: $F_2=N_2 i_{12}$

$$F_1+F_2=F_m \quad N_1 i_{1L}+N_2 i_{12}=0$$

$$i_{1L} = -\frac{N_2}{N_1} i_2$$

$$\dot{F}_1 + \dot{F}_2 = \dot{F}_m$$

$$N_1 \dot{I}_1 + N_2 \dot{I}_2 = N_1 \dot{I}_m$$

MMF Equation

Leakage flux and Leakage reactance

$$e_{1\sigma} = -N_1 \frac{d\phi_{1\sigma}}{dt} = -N_1 \frac{d(N_1 \mathbf{i}_1 \cdot \Lambda_{1\sigma})}{dt} = -N_1^2 \Lambda_{1\sigma} \frac{d\mathbf{i}_1}{dt}$$

$$L_{1\sigma} = N_1^2 \Lambda_{1\sigma} \quad \boxed{e_{1\sigma} = -L_{1\sigma} \frac{d\mathbf{i}_1}{dt}} \quad X_{1\sigma} = \omega L_{1\sigma} \quad \boxed{\dot{E}_{1\sigma} = -jX_{1\sigma} \dot{\mathbf{I}}_1}$$

$$e_{2\sigma} = -N_2 \frac{d\phi_{2\sigma}}{dt} = -N_2 \frac{d(N_2 \mathbf{i}_2 \cdot \Lambda_{2\sigma})}{dt} = -N_2^2 \Lambda_{2\sigma} \frac{d\mathbf{i}_2}{dt}$$

$$L_{2\sigma} = N_2^2 \Lambda_{2\sigma} \quad \boxed{e_{2\sigma} = -L_{2\sigma} \frac{d\mathbf{i}_2}{dt}} \quad X_{2\sigma} = \omega L_{2\sigma} \quad \boxed{\dot{E}_{2\sigma} = -jX_{2\sigma} \dot{\mathbf{I}}_2}$$

Voltage Equation

$$u_1 + e_1 + e_{1\sigma} = i_1 R_1$$

$$u_1 = i_1 R_1 - e_{1\sigma} - e_1$$

$$u_1 = i_1 R_1 + L_{1\sigma} \frac{di_1}{dt} - e_1$$



$$\dot{U}_1 = \dot{I}_1 R_1 + \underline{j\dot{I}_1 X_{1\sigma}} - \dot{E}_1$$

$$\dot{U}_1 = \dot{I}_1 (R_1 + jX_{1\sigma}) - \dot{E}_1$$

$$Z_{1\sigma} = R_1 + jX_{1\sigma}$$

$$e_2 + e_{2\sigma} = i_2 R_2 + u_2$$

$$e_2 = i_2 R_2 - e_{2\sigma} + u_2$$

$$e_2 = i_2 R_2 + L_{2\sigma} \frac{di_2}{dt} + u_2$$



$$\dot{E}_2 = \dot{I}_2 R_2 + jX_{2\sigma} \dot{I}_2 + \dot{U}_2$$

$$\dot{E}_2 = \dot{I}_2 (R_2 + jX_{2\sigma}) + \dot{U}_2$$

$$Z_{2\sigma} = R_2 + jX_{2\sigma}$$

Basic Equation of Transformer

$$\dot{U}_1 = \dot{I}_1 Z_{1\sigma} - \dot{E}_1$$

$$\dot{E}_2 = \dot{I}_2 Z_{2\sigma} + \dot{U}_2$$

$$\frac{\dot{E}_1}{\dot{E}_2} = k$$

$$N_1 \dot{I}_1 + N_2 \dot{I}_2 = N_1 \dot{I}_m$$

$$\dot{E}_1 = -\dot{I}_m Z_m$$

Winding Referring

Original



Referred

N_2

N_1

$$N_1 \dot{I}'_2$$

=

$$N_2 \dot{I}_2$$



$$\dot{I}'_2 = \frac{N_2}{N_1} \dot{I}_2 = \frac{1}{k} \dot{I}_2$$

$$\dot{E}'_2 = -N_1 \frac{d\phi}{dt} = \dot{E}_1 = k \dot{E}_2$$

Impedance Referring

$$I_2'^2 R_2' = I_2^2 R_2 \quad \rightarrow \quad R_2' = \left(\frac{I_2}{I_2/k} \right)^2 R_2 = k^2 R_2$$

$$I_2'^2 X_{2\sigma}' = I_2^2 X_{2\sigma} \quad \rightarrow \quad X_{2\sigma}' = \left(\frac{I_2}{I_2/k} \right)^2 X_{2\sigma} = k^2 X_{2\sigma}$$

Original

$$\dot{U}_1 = \dot{I}_1 Z_{1\sigma} - \dot{E}_1$$

$$\dot{E}_2 = \dot{I}_2 Z_{2\sigma} + \dot{U}_2$$

$$\frac{\dot{E}_1}{\dot{E}_2} = k$$

$$N_1 \dot{I}_1 + N_2 \dot{I}_2 = N_1 \dot{I}_m$$

$$\dot{E}_1 = -\dot{I}_m Z_m$$

Referred


$$\dot{U}_1 = \dot{I}_1 Z_{1\sigma} - \dot{E}_1$$

$$\dot{E}'_2 = \dot{I}'_2 Z'_{2\sigma} + \dot{U}'_2$$

$$\dot{I}_1 + \dot{I}'_2 = \dot{I}_m$$

$$\dot{E}_1 = \dot{E}'_2 = -\dot{I}_m Z_m$$


Equivalent Circuits

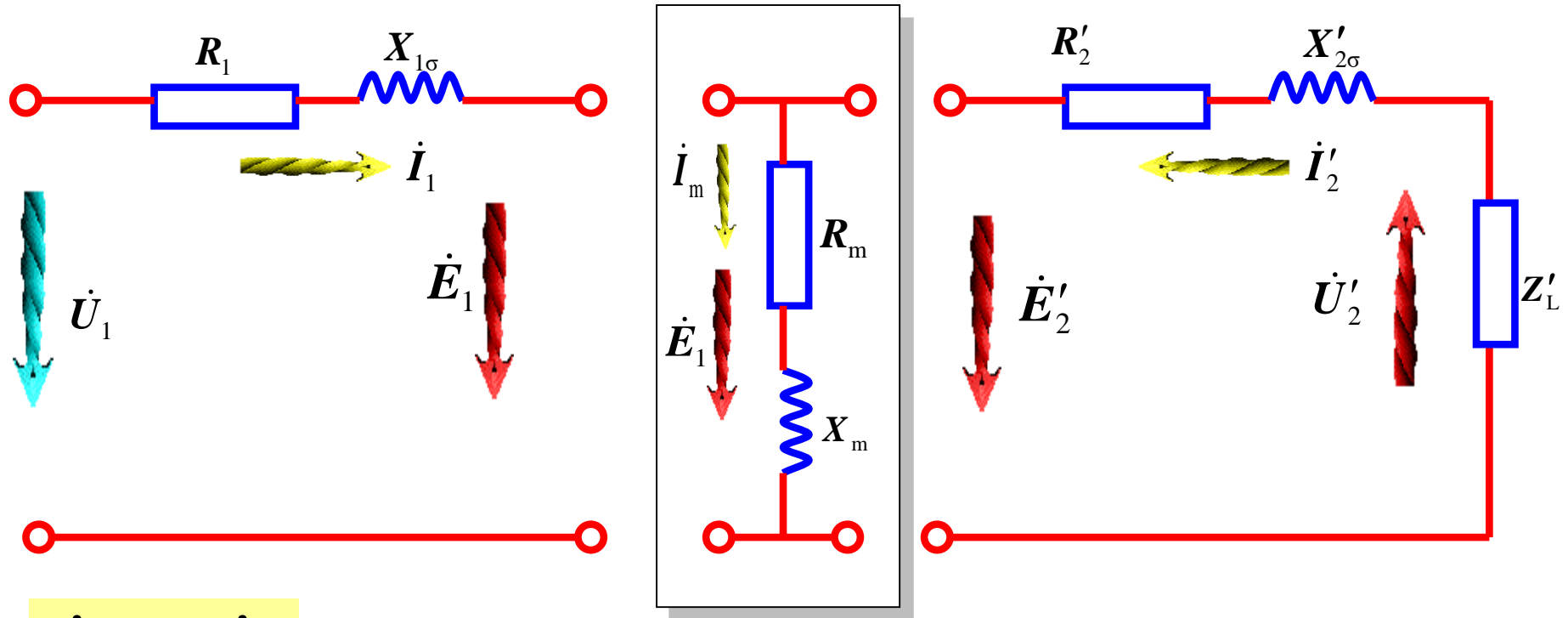

$$\dot{E}_1 = \dot{E}'_2$$

$$\dot{I}_1 + \dot{I}'_2 = \dot{I}_m$$

Equivalent Circuits

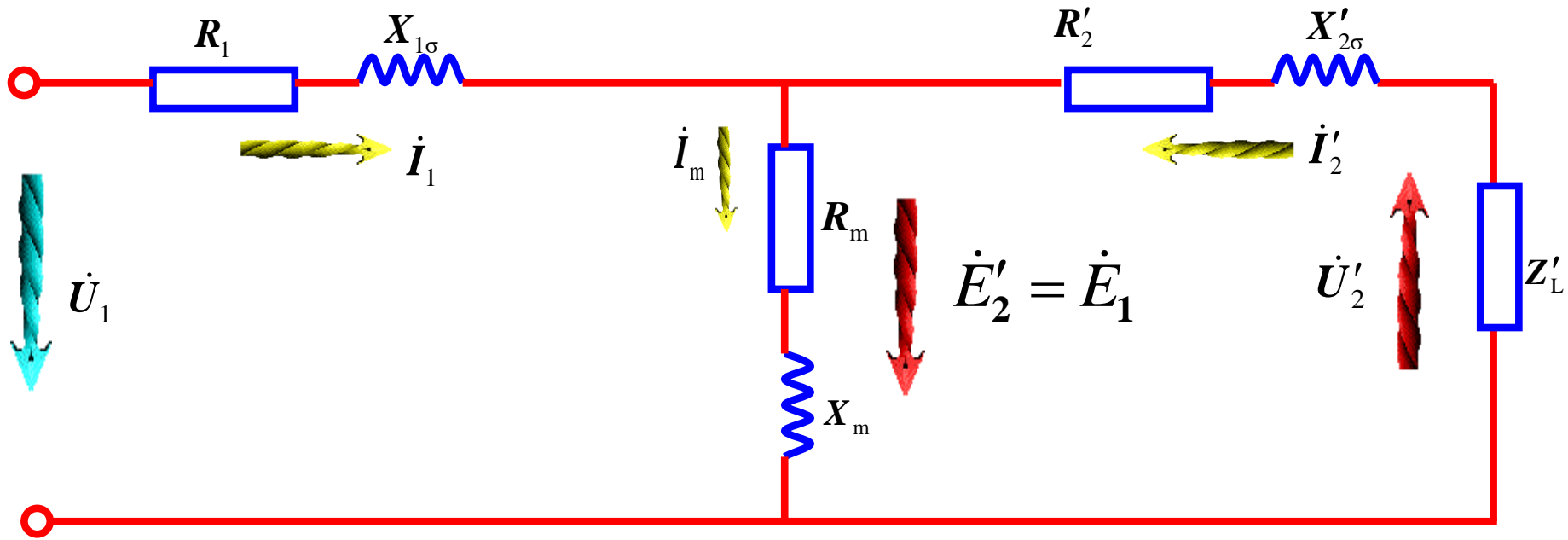


Simplified Equivalent Circuits


$$R_k = R_1 + R'_2$$

$$X_k = X_{1\sigma} + X'_{2\sigma}$$
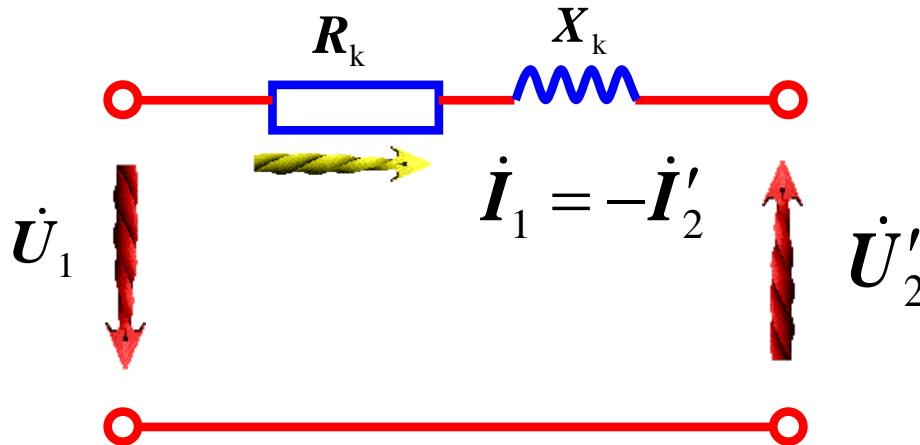
$$Z_k = Z_{1\sigma} + Z'_{2\sigma} = R_k + jX_k$$



Equivalent Circuits

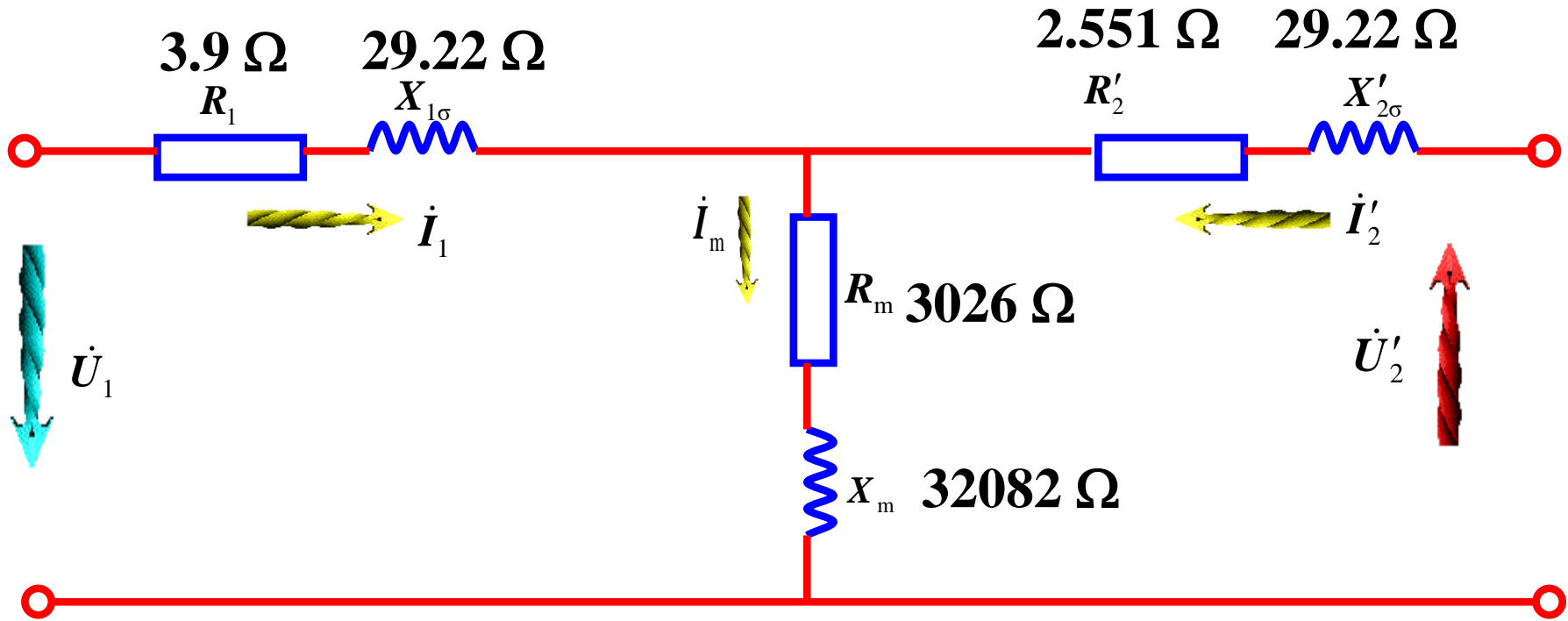


$$S_N = 20000 \text{ kVA}$$

$$U_{1N} / U_{2N} = 127 \text{ kV} / 11 \text{ kV}$$

$$I_{1N} = 157.5 \text{ A} \quad I_{2N} = 1818 \text{ A}$$

If 220V is applied to the high-voltage side of a $U_{1N}/U_{2N}=220\text{V}/110\text{V}$ single-phase transformer, the exciting current is 0.3A and the no-load loss is 4W. Calculate the exciting current and the no-load loss if

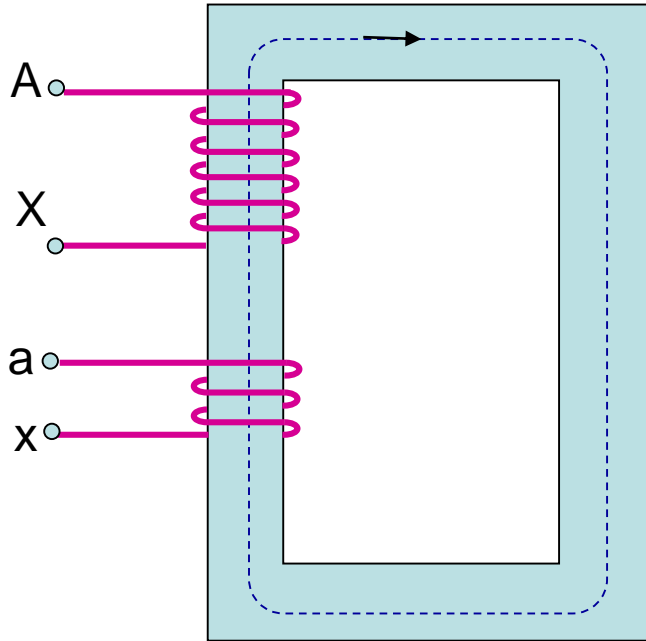- the terminal X is connected to the terminal a and 330V is applied to the high-voltage side (terminal A and x) of the transformer ;
- the terminal X is connected to the terminal x and 110V is applied to the high-voltage side (terminal A and a) of the transformer.



Per-Unit Value

$$\text{Per-Unit Value} = \frac{\text{Practice Value}}{\text{Base Value}}$$

Base Value	Primary	Secondary
Voltage	$U_{1b} = U_{1N}$	$U_{2b} = U_{2N}$
Current	$I_{1b} = I_{1N}$	$I_{2b} = I_{2N}$
Impedance	$Z_{1b} = U_{1N} / I_{1N}$	$Z_{2b} = U_{2N} / I_{2N}$
Power	$S_{1b} = S_{1N}$	$S_{2b} = S_{2N}$

Advantages of Per-Unit Value

$$Z_k^* \approx 0.03 \sim 0.1$$

$$I_{1N}^* = U_{1N}^* = I_{2N}^* = U_{2N}^* = 1$$

$$I_0^* \approx 0.02 \sim 0.05$$

$$P_N^* = \frac{P_N}{S_N} = \frac{S_N \cos \varphi}{S_N} = \cos \varphi$$

$$Q_N^* = \frac{Q_N}{S_N} = \frac{S_N \sin \varphi}{S_N} = \sin \varphi$$

$$Z_k^* = \frac{Z_k}{Z_{1b}} = \frac{(I_{1N} Z_k)}{U_{1N}} = u_k$$

$$U_2'^* = \frac{U_2'}{U_{1b}} = \frac{k U_2}{U_{1N}} = \frac{U_2}{U_{1N}/k} = \frac{U_2}{U_{2N}} = \frac{U_2}{U_{2b}} = U_2^*$$

Advantages of Per-Unit Value

$$I_2^* = 0: \text{ (No Load)}$$

$$I_2^* = 1: \text{ (Full Load)}$$

$$I_2^* = 0.5: \text{ (Half Load)}$$



$$I_2^* = 0.7: \text{ (Under Load)}$$

$$I_2^* = 1.2: \text{ (Over Load)}$$

Operation Performances

External Characteristic


What we desire: What the practice:

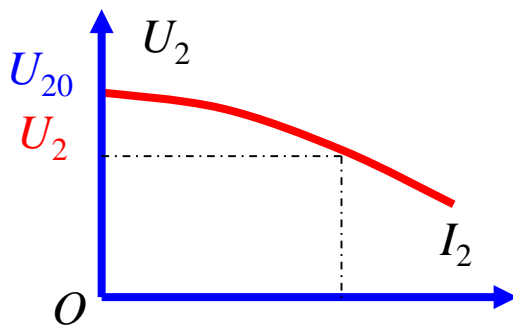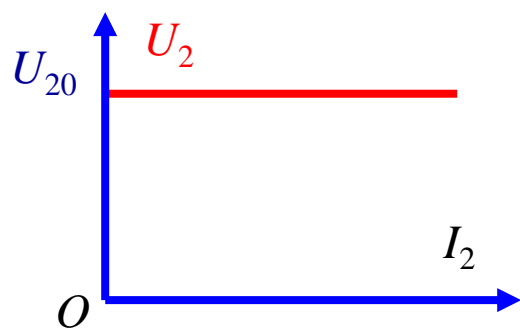

When $U_1=U_{1N}$ and $\cos\phi=C$, find $U_2=f(I_2)$

Voltage Regulation
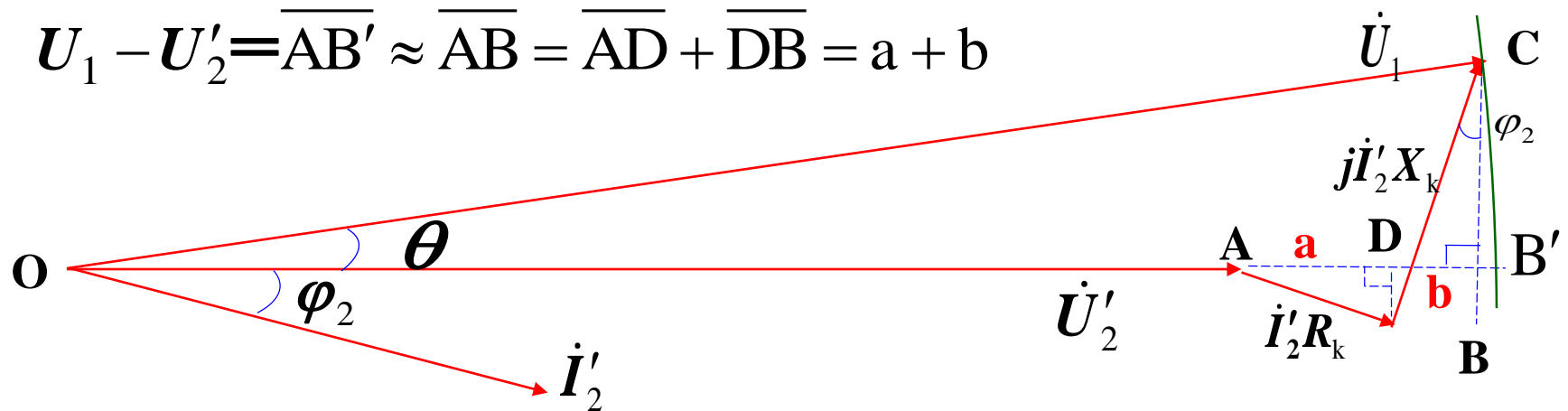
$$\Delta u = \frac{U_{20} - U_2}{U_{2N\phi}} \times 100\% = \frac{U_{1N\phi} - U'_2}{U_{1N\phi}} \times 100\%$$




$$a = I'_2 R_k \cos \varphi_2 \quad b = I'_2 X_k \sin \varphi_2$$

$$\Delta u = \frac{U_{1N\phi} - U'_2}{U_{1N\phi}} \times 100\% \approx \frac{I'_2 R_k \cos \varphi_2 + I'_2 X_k \sin \varphi_2}{U_{1N\phi}} \times 100\%$$

$$= \frac{I'_2 R_k \cos \varphi_2 + I'_2 X_k \sin \varphi_2}{I_{1N\phi} (U_{1N\phi} / I_{1N\phi})} \times 100\%$$

$$\Delta u = I^* (R_k^* \cos \varphi_2 + X_k^* \sin \varphi_2) \times 100\%$$
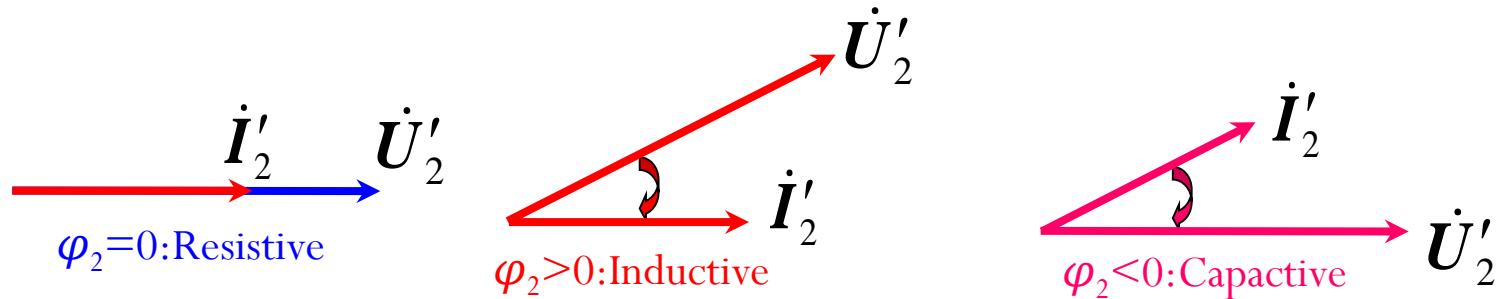
$$\Delta u = I^* (R_k^* \cos \varphi_2 + X_k^* \sin \varphi_2) \times 100\%$$





Voltage regulation is

- 1. related to the load current I_2^* ,**
- 2. related to the short-circuited impedance Z_k^* , and**
- 3. related to the load property $\cos \varphi_2$.**

Tap switch




Efficiency Characteristic

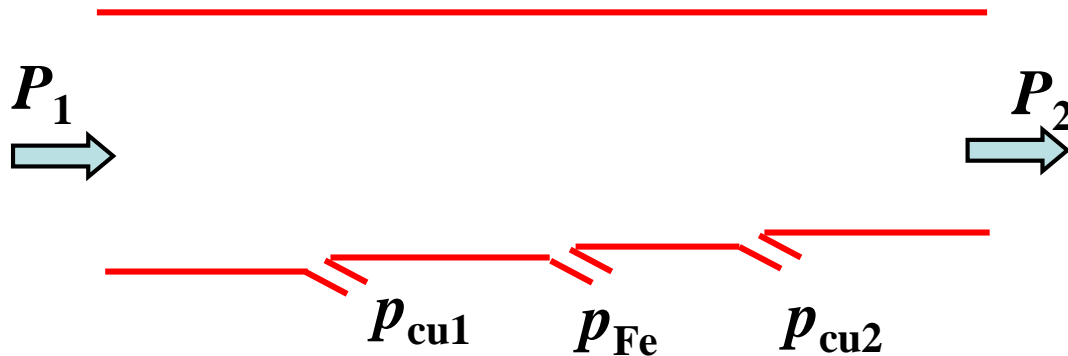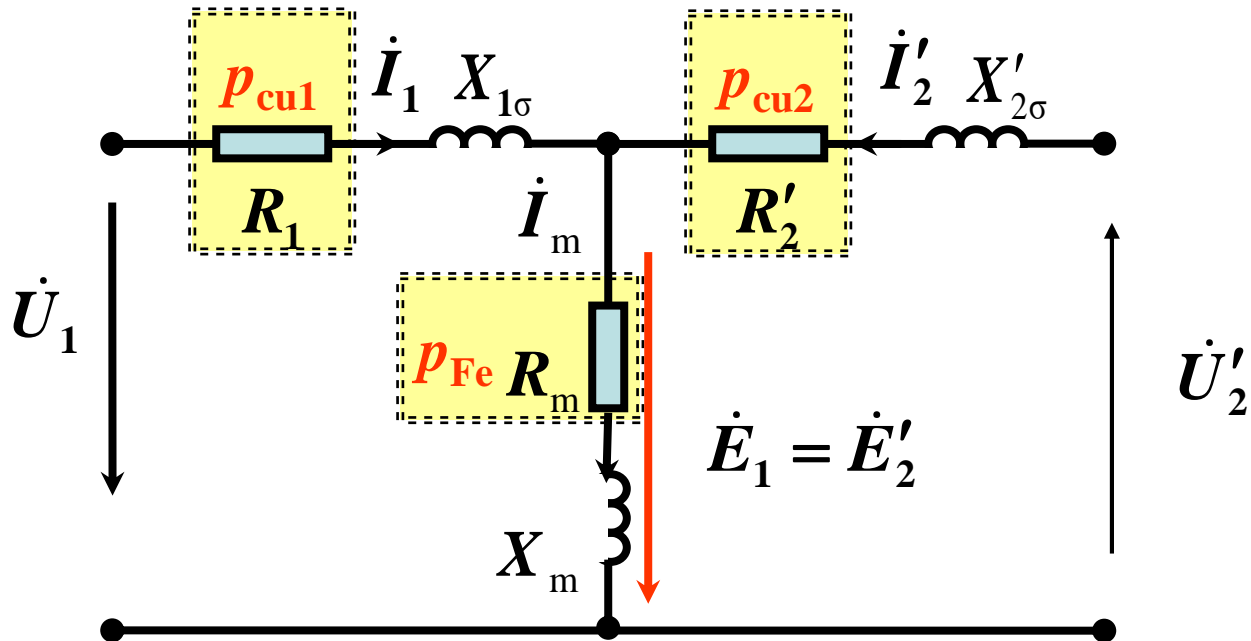

$$\eta = 1 - \frac{\sum p}{P_2 + \sum p} = 1 - \frac{p_0 + p_k}{P_2 + p_0 + p_k}$$
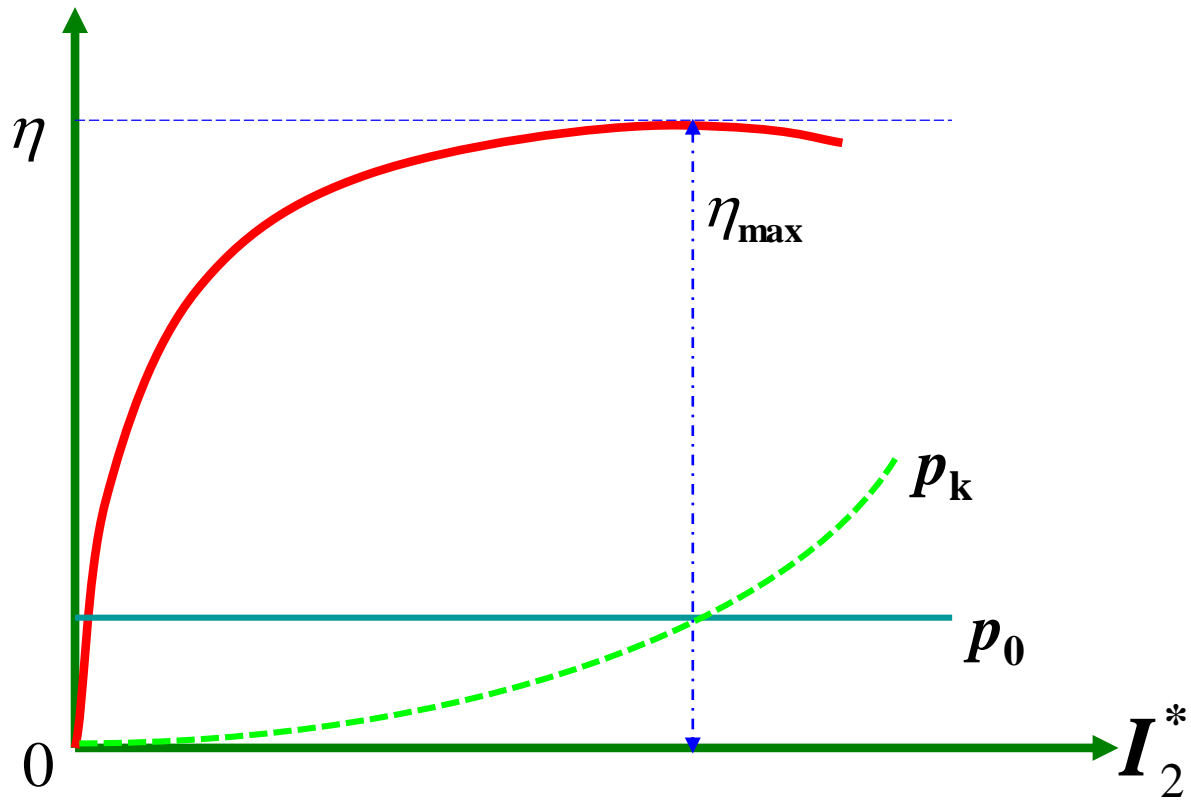
$$\eta = 1 - \frac{p_0 + I_2^{*2} p_{kN}}{S_N I_2^* \cos \varphi_2 + p_0 + I_2^{*2} p_{kN}}$$




When $\frac{d\eta}{dI_2^*} = 0$, that is $I_2^* = \sqrt{\frac{p_0}{p_{kN}}}$:

$$p_k = I_2^{*2} p_{kN} = \left(\sqrt{\frac{p_0}{p_{kN}}} \right)^2 p_{kN} = p_0$$


Parallel operation



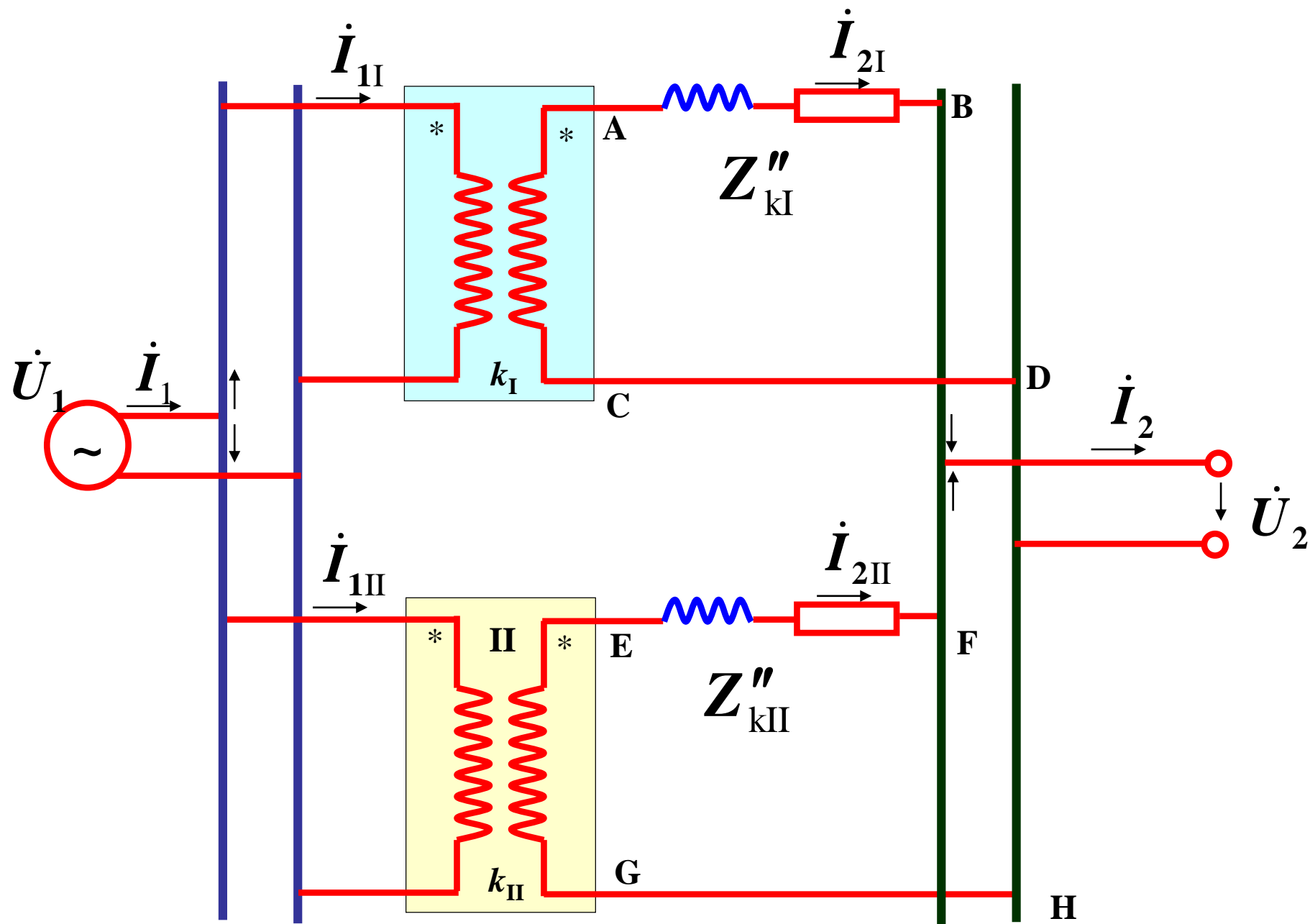


Parallel operation
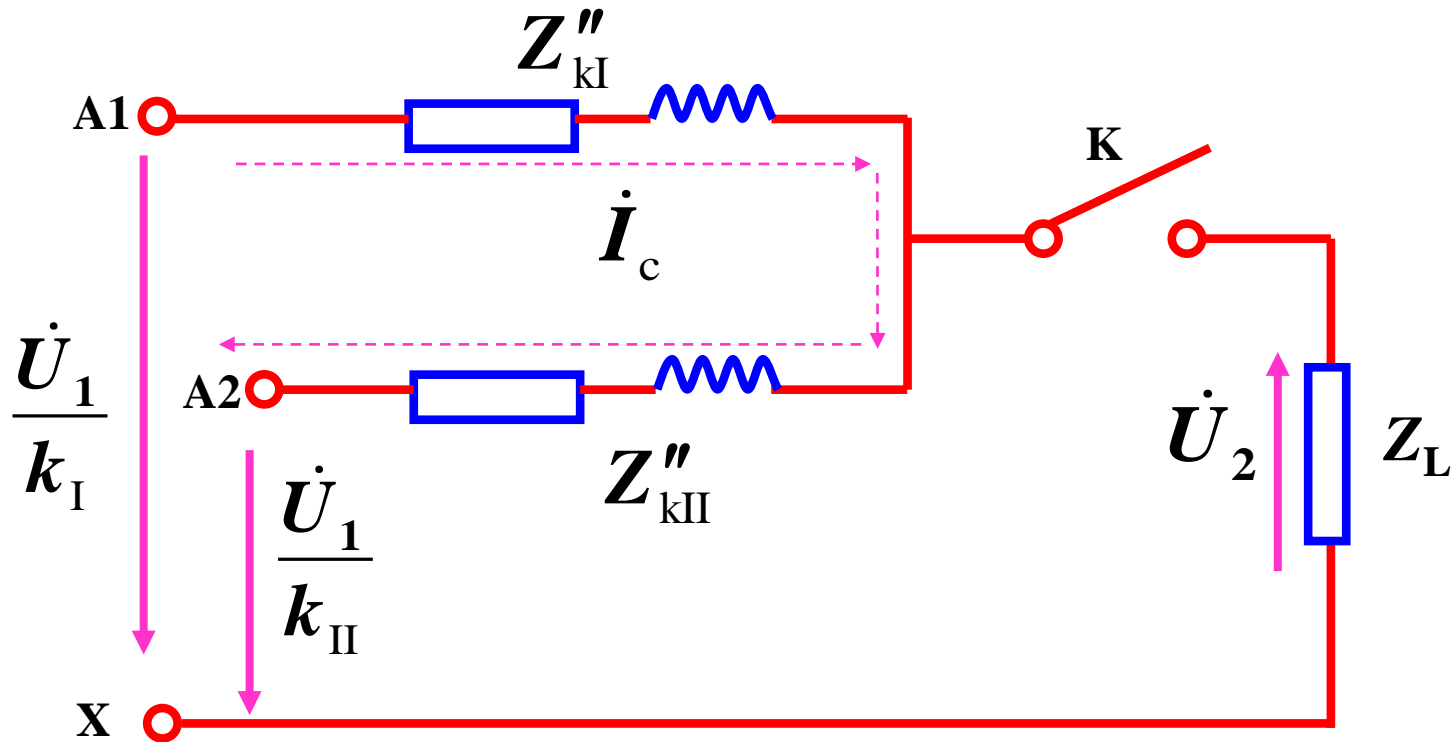
$$\dot{I}_c = \frac{\frac{\dot{U}_1}{k_I} - \frac{\dot{U}_1}{k_{II}}}{Z''_{kI} + Z''_{kII}}$$




Parallel operation

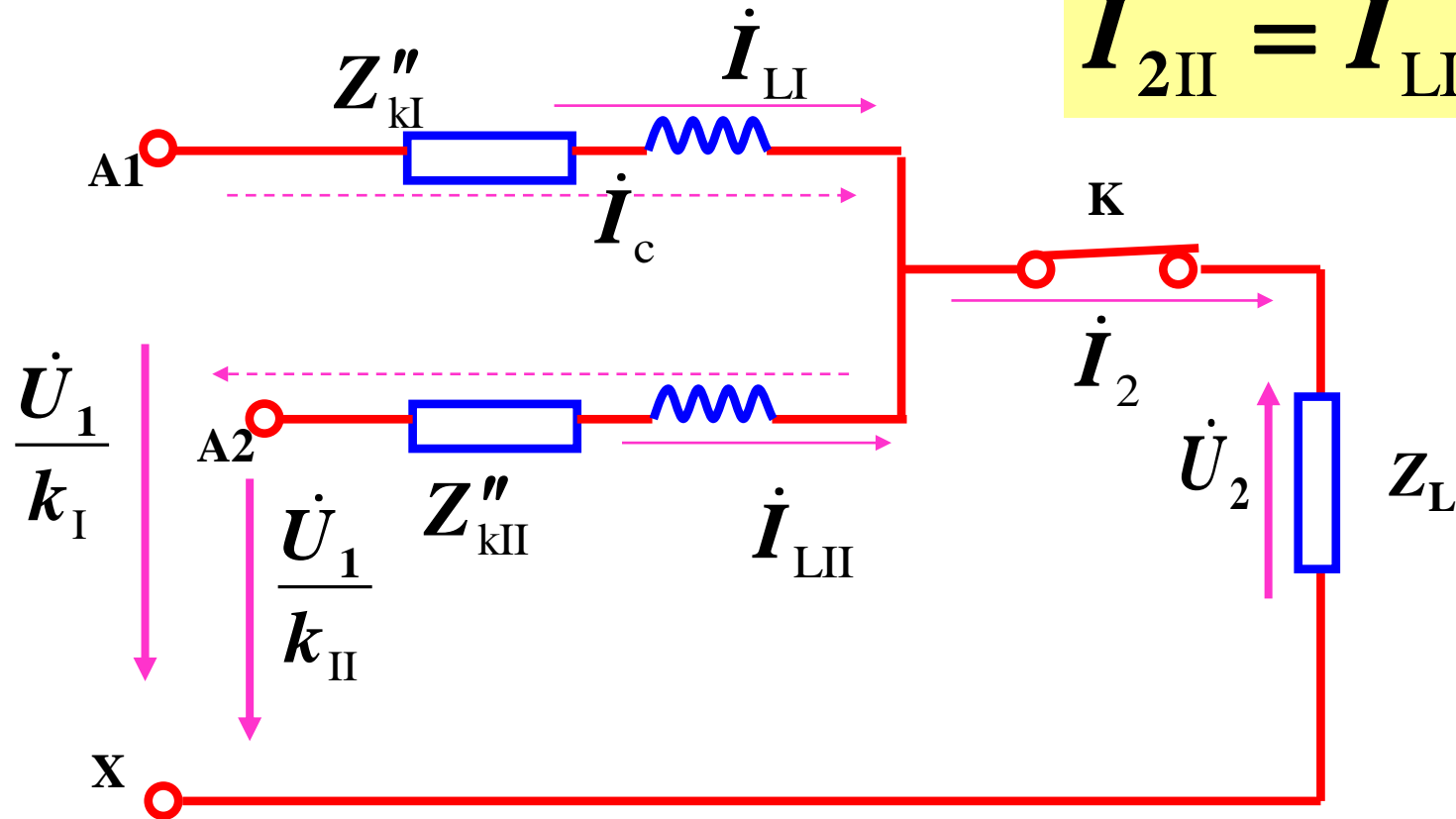

$$\dot{I}_{2I} = \dot{I}_{LI} + \dot{I}_c$$

$$\dot{I}_{2II} = \dot{I}_{LII} - \dot{I}_c$$

Parallel operation

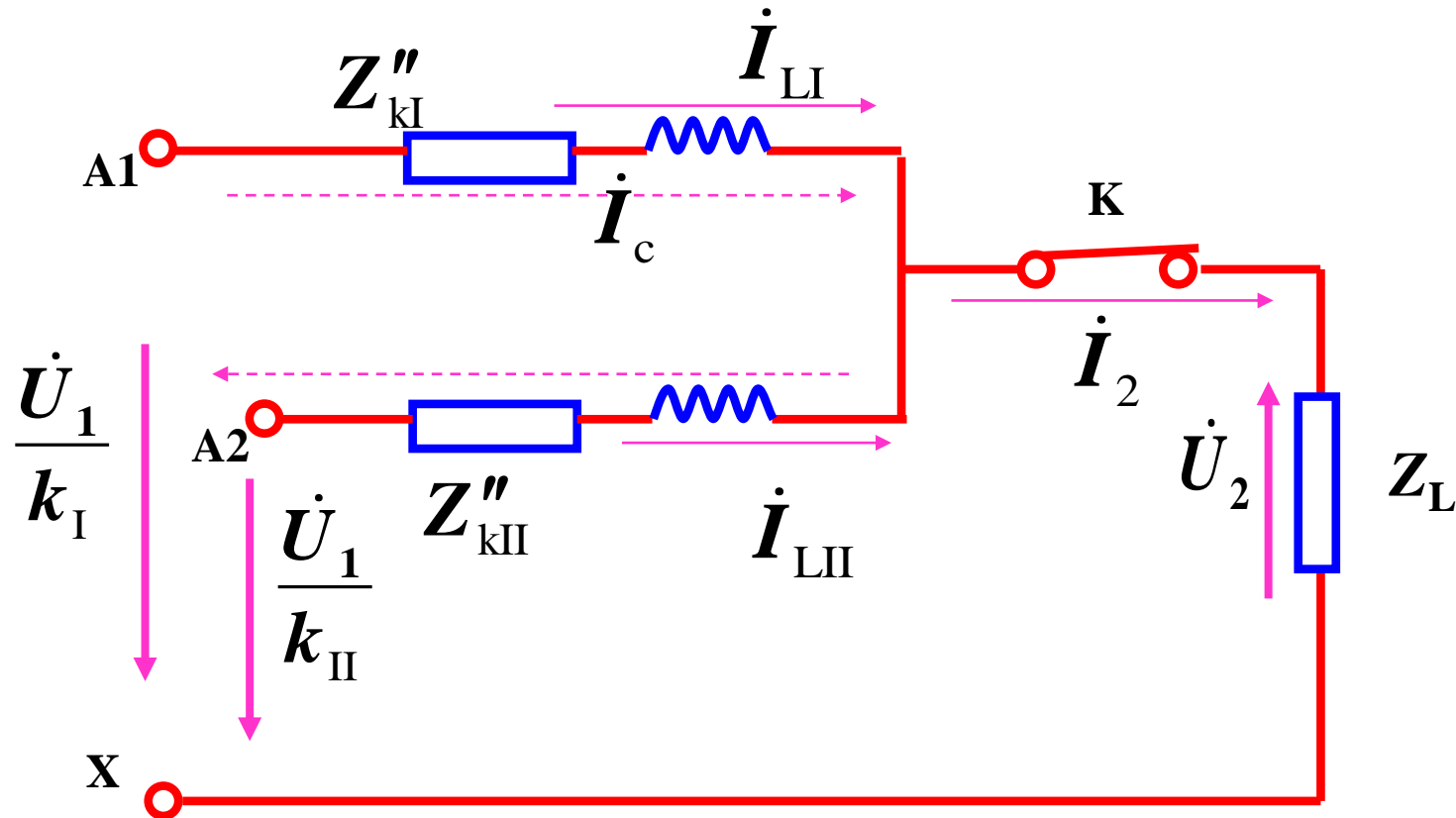

$$\dot{I}_{LI} + \dot{I}_{LII} = \dot{I}_2$$

$$\dot{I}_{LI} Z''_{kI} = \dot{I}_{LII} Z''_{kII}$$

For two same single-phase transformers with the voltage ratio of $U_{IN}/U_{2N}=220V/110V$, any one of them has a no-load current of 0.6A and a no-load loss of 10W if 220V is applied to the primary side at no-load operation. Calculate the total no-load current and the no-load loss if

- (a) 440V is applied to the primary side with the primary terminals of two transformers are connected in series;**
- (b) 220V is applied to the primary side with the primary terminals of two transformers are connected in parallel.**